

Year 4 Science -Term 3 Week 1 Lesson 2

How Switches Work

LO: To Understand and explain how a switch works.

Fill in the missing words.

off

breaks

on

flow

electrons

stop

complete

A switch _____ a complete circuit on purpose to _____ the flow of _____ when it is _____.

When the switch is _____, the circuit is _____ and so the electrons are able to _____ around the circuit.

