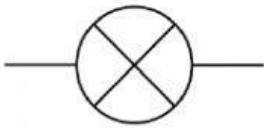
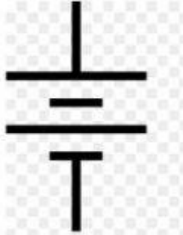


Name: _____ Date: _____

SCIENCE WORKSHEETS: PARTS OF AN ELECTRICAL CIRCUIT

Word Bank

What part? *Battery,* *lamp,* *switch,* *wire,*

	Symbol!	Which part?
		_____
		_____
		_____
		_____