

Name: \_\_\_\_\_

Class: \_\_\_\_\_

Date: \_\_\_\_\_


### Exercise 5.4 Switches

1. Complete the sentences by choosing the correct answer from the choices.

The switch turns the electric \_\_\_\_\_ on or off. It is the same idea as turning a tap on or off.

\_\_\_\_\_ a switch completes a circuit and allows electric current to flow.

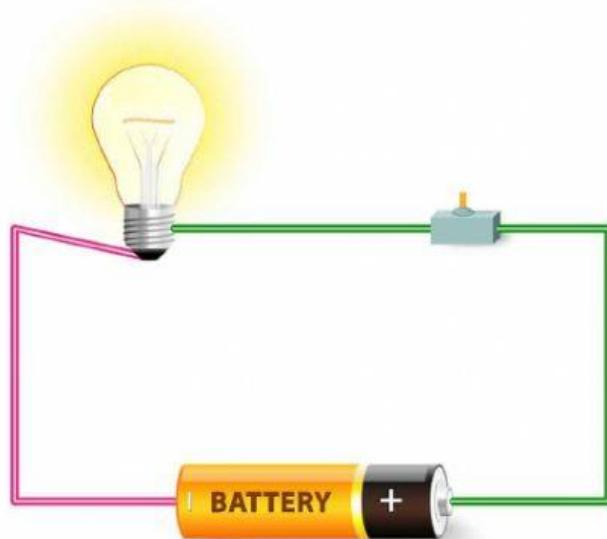\_\_\_\_\_ the switch breaks the circuit.



2. Kinds of Switches. Match the picture of the switch to its correct name.

