

Name: _____ Class: _____ Date: _____

CHECK YOUR PROGRESS

1. These have two names. What are they?



2. What are these called?








3. Will the bulb be ON or OFF in these circuits?




ON

OFF

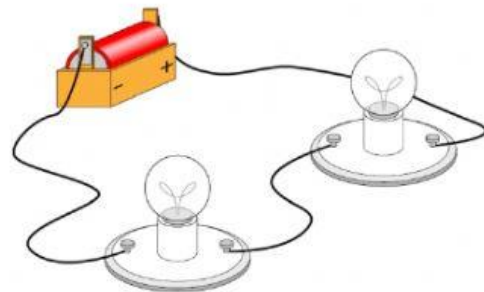


ON

OFF

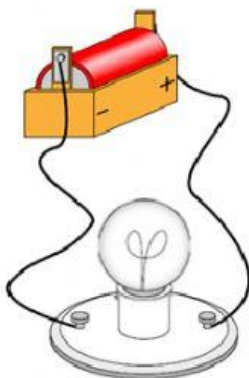

ON


OFF

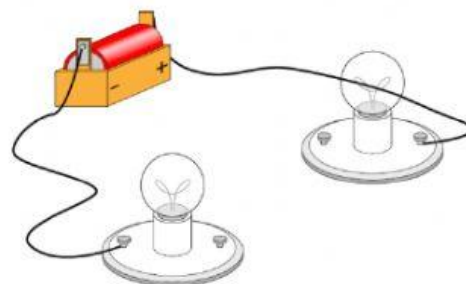

ON


OFF

4. Will these circuits work?

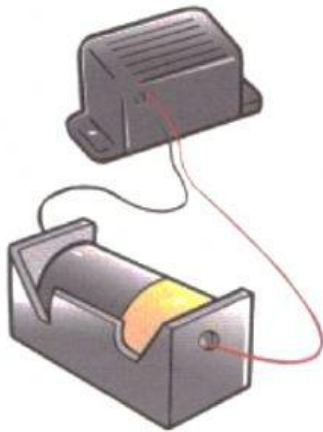


YES

NO

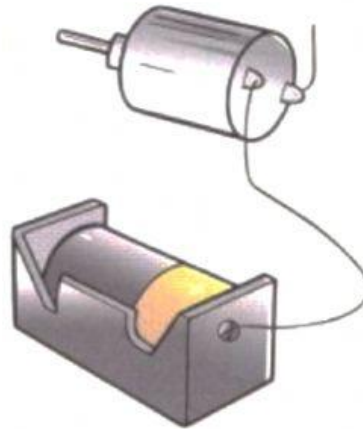

YES

NO

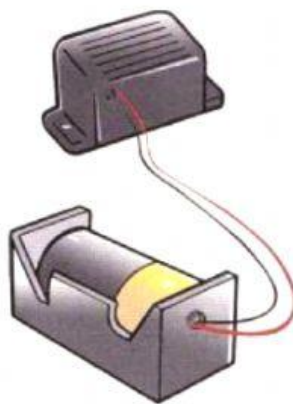

YES

NO