

NAME: \_\_\_\_\_ GRADE 1- \_\_\_\_\_ DATE: \_\_\_\_\_

LO: I can identify the components of a simple circuit.


TASK 1: Complete the statements about the components of simple circuit. Choose your answer from the box.

| Conductor | Source | Circuit | Load |
|-----------|--------|---------|------|
|-----------|--------|---------|------|

1. \_\_\_\_\_ is a complete path around which electricity can flow.
2. \_\_\_\_\_ it provides electrical energy or power. Battery is an example of this component.
3. \_\_\_\_\_ it allows electric current to pass through. Wire is an example of this component.
4. \_\_\_\_\_ it uses or consumes the power or energy. Bulb is an example of this component.

TASK 2: Label the components of a simple circuit.

- Battery
- Wire
- Bulb

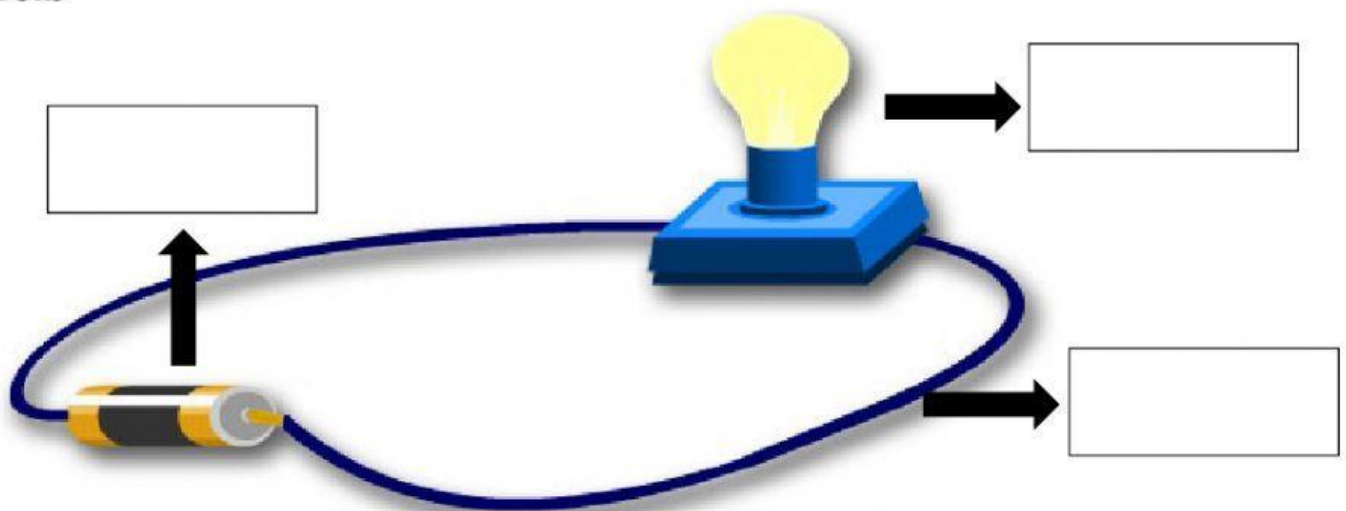

TASK 3: Match the following. Draw a line.

- |              |            |
|--------------|------------|
| 1. Conductor | a. Bulb    |
| 2. Load      | b. Battery |
| 3. Source    | c. Wire    |