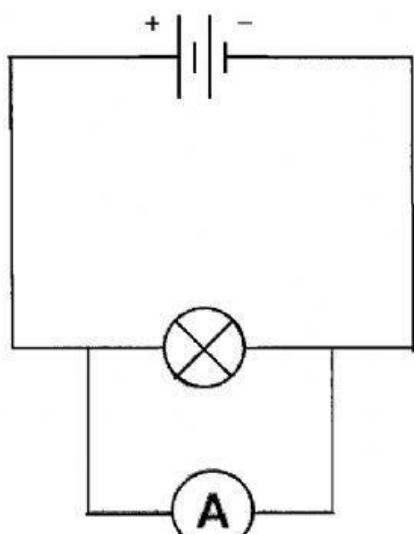


6. Which statement about electric current is correct?


- it always flows clockwise
- it gets used up as it goes around the circuit
- it does not get used up as it goes around the circuit

7. What is wrong with this circuit diagram?



- there is only one lamp
- the ammeter should be connected along the series path
- the ammeter should be connected across the path to make a parallel circuit

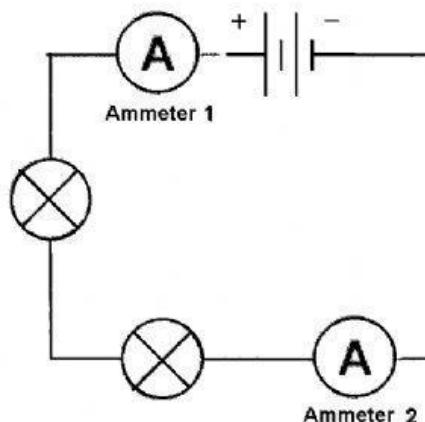8. Which ammeter will have the biggest reading?



- ammeter 1
- ammeter 2
- they will read the same