
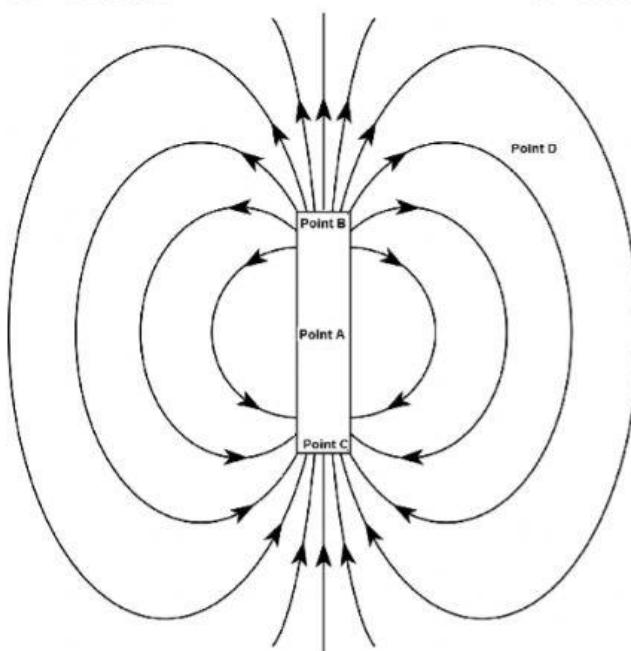


## Multiple Response

*Identify one or more choices that best complete the statement or answer the question.*


## ***Series and Parallel Circuits***

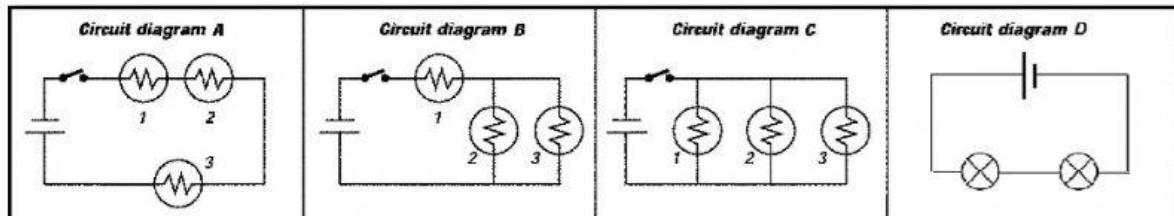

44. At which point or points would the magnetic force be the weakest? Pick all that apply.

- a. Point A
- b. Point B
- c. Point C
- d. Point D

### **Series and Parallel Circuits**

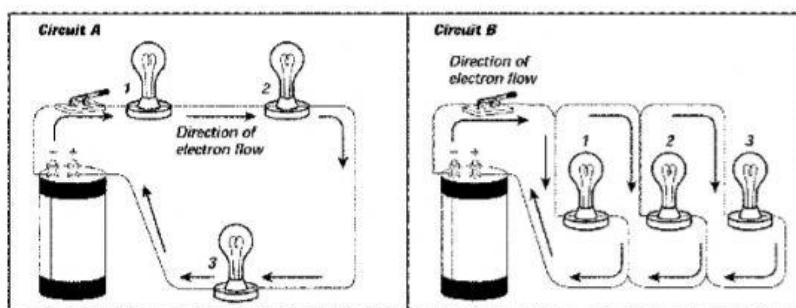

45. Pick all the statements that are true.

- a. Circuit B is a series circuit
- b. Circuit B is a parallel circuit
- c. Circuit A is a series circuit
- d. Circuit A is a parallel circuit