

SCIENCE EXERCISE 3

Bismillaahirrohmaanirrohiim

Fill in the blanks by using the helping words.

batteries	fires	burns	buzzers	watches
electricity	care	circuit	Shocks	wires
bulbs	mains	kettles	switches	toasters

1. Electricity comes from the _____ and _____ or cells.
2. Electricity from the main is used by things such as:
 - Electric _____
 - Electric _____
3. Electricity from battery is used by things such as:
 - Toy cars
 - _____
4. Electricity flows through a path called a _____, which may be made up of:
 - Cells or batteries that push _____ around the circuit.
 - _____ that close or open the circuit.
 - _____ that connect parts of the circuit.
 - _____ that use electricity to give off light.
 - _____ that use electricity to make sounds.
5. Electricity must be use with _____ as it can cause:
 - Electric _____
 - _____
 - _____

Alhamdulillahirobbil'alamiin