

Electrical symbols

Name_____ Class_____ Date_____

Match the part with its electrical circuit symbol.

Name
ammeter
cell
bulb
switch
wire
fuse
voltmeter
motor

Symbol







