


Identificar Tipos de Circuitos



Circuito Serie



Circuito Cerrado

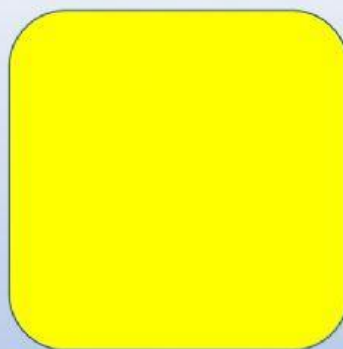

Circuito Paralelo



Circuito Abierto

