

7.1 Electric Circuit

A Name the components found in the electrical circuit below.

SP 7.1.1

Dry cell

Bulb

Switch


Connecting
wire

1.

2.

3.

4.

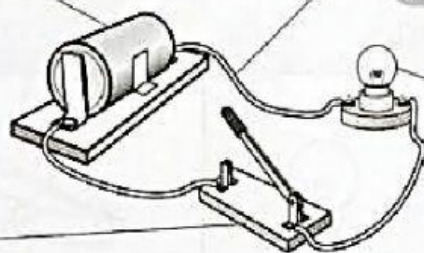


B Match the electrical component to its function.



Complete and break an
electric circuit.

Supply electrical energy

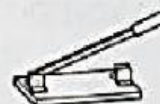

Produce light



Connect each electrical
component into a
complete circuit

