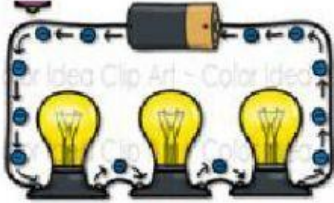
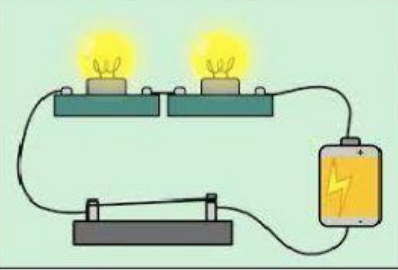
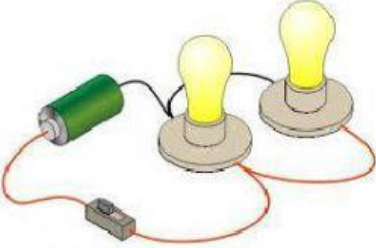
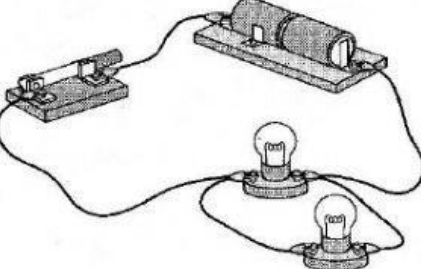


Name :

Class :

Name the circuit below correctly, series circuit or parallel circuit.

1.		2.	
3.		4.	
5.		6.	
7.		8.	