

Nama:

Kelas:

SUIS MIKRO

1. Apakah fungsi suis mikro

- Sebagai dan
bergantung kepada

2. Nyatakan maksud COM, NC dan NO pada kaki suis mikro



3. Lengkapkan keterangan berkaitan suis mikro dibawah

A circuit diagram showing a battery connected to a micro switch. The COM terminal is connected to the positive terminal of the battery. The NO terminal is connected to the positive terminal of a bulb labeled 'Mentol 1'. The NC terminal is connected to the positive terminal of a bulb labeled 'Mentol 2'. The negative terminal of the battery is connected to the common ground of the bulbs.	i) Wayar suis mikro disambung pada kaki COM dan ii) Apabila suis mikro ditekan, mentol 1 dan 2 akan
A circuit diagram showing a battery connected to a micro switch. The COM terminal is connected to the positive terminal of the battery. The NO terminal is connected to the positive terminal of a bulb labeled 'Mentol 1'. The NC terminal is connected to the positive terminal of a bulb labeled 'Mentol 2'. The negative terminal of the battery is connected to the common ground of the bulbs.	i) Wayar suis mikro disambung pada kaki COM dan ii) Apabila suis mikro ditekan, mentol 1 dan 2 akan

Nama:

Kelas: