

Circuits

Fill in the missing words

loop

complete

energy

path

negative

positive

electricity

A circuit is a _____ that allows _____
to pass through it.

Electricity always travels from the _____
to the _____.

A circuit will only work if it is _____. This
means it must make a complete _____, otherwise the
electrical _____ cannot flow.

Draw arrows on the diagram to show which way round the electricity is flowing.

