

Label the electrical components in the circuit below.

bulb


connecting wire

switch

dry cell

1.

2.

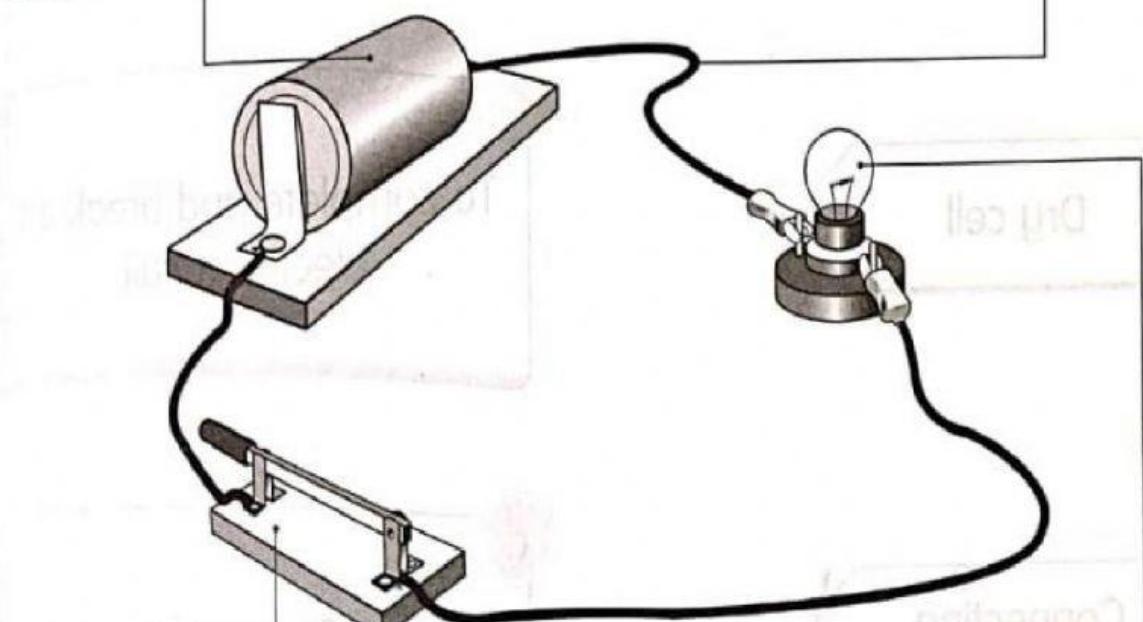

4.

3.