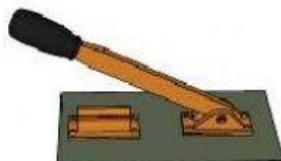


Match the pictures to their functions.



Complete
and break the
electric circuit



Supply
electrical
energy



Connect
components
in the electric
circuit



Produce light