

Electricity

A. Answer all question.

wire	dry cell	torch light	main electricity
washing machine	watch	dry cell	light bulb

1. There are two different sources of electricity .

They are

and

2. One example of appliance that uses main electricity

is a

3. Some electric appliance that use dry cell is a

4. A simple circuit can have three component. There are


, and

Science Year 3

B. Type the correct name for each of the electric component of a simple circuit.



C. Choose the correct answer.

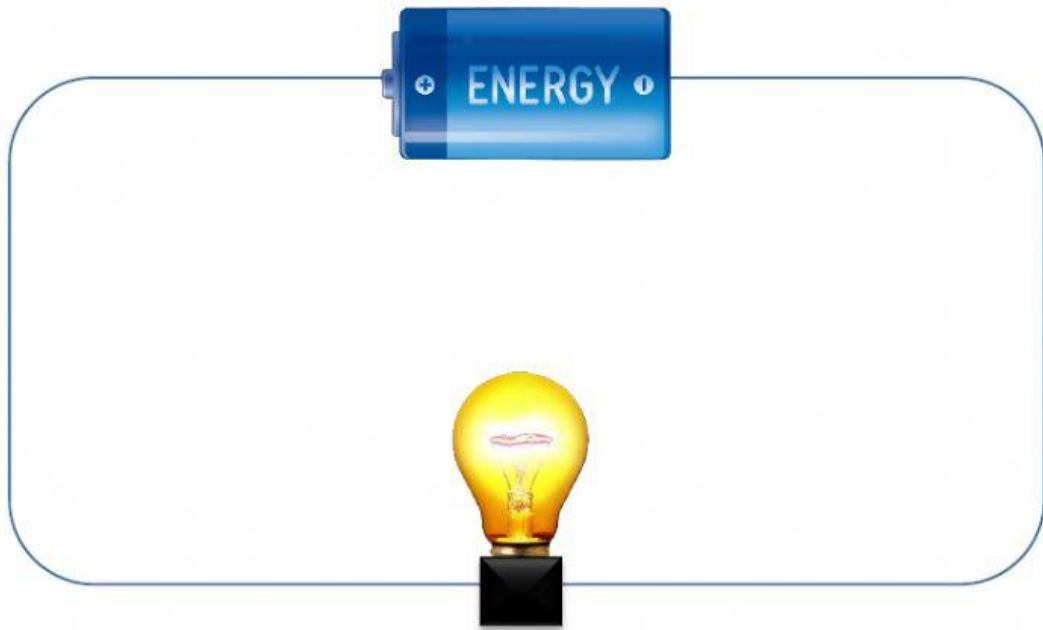

1. What do you call this circuit?

2. Why?