



WORKSHEETS



For the Prathomsueksa 6 students of Bangkulad School

Name: _____ Room: _____ Number: _____

A. Click COMPLETE if the sentence is about a complete circuit and INCOMPLETE if the sentence is about an incomplete circuit.

1. The switch is turned on. **COMPLETE** **INCOMPLETE**
2. Electricity can not flow. **COMPLETE** **INCOMPLETE**
3. It is also called an open circuit. **COMPLETE** **INCOMPLETE**
4. The bulb lights up. **COMPLETE** **INCOMPLETE**

B. Match the words in column A to the symbols in Column B. Connect them by drawing lines.

COLUMN A

5. on switch
6. connecting wire
7. battery
8. off switch
9. bulb
10. simple electric circuit

COLUMN B

