

Name _____ Date _____

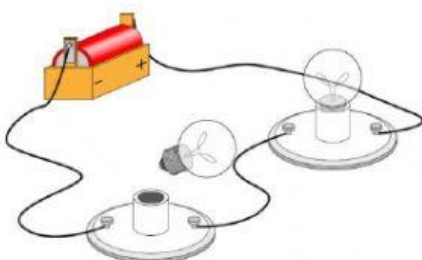
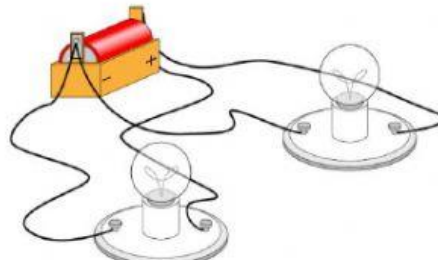
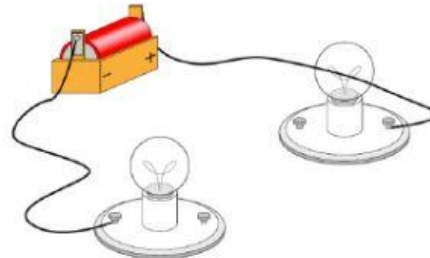
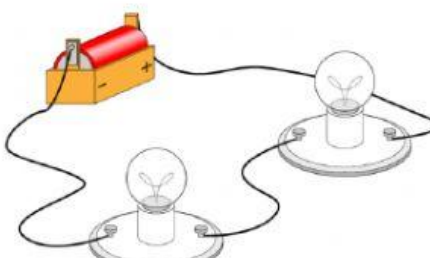
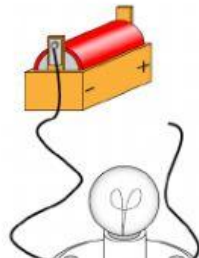
LO – To be able to work with electrical circuits

AC 1.2 Identify simple circuits in which electricity can flow


AC 3.1 – To build simple working circuits

Instructions:

1. Make a prediction on whether the circuit will work
2. Build the circuit and check your prediction


1. Will it work? YES NO  Did it work? YES NO	2. Will it work? YES NO  Did it work? YES NO
3. Will it work? YES NO  Did it work? YES NO	4. Will it work? YES NO  Did it work? YES NO
5. Will it work? YES NO  Did it work? YES NO	6. Will it work? YES NO  Did it work? YES NO

7. Will it work? **YES** **NO**

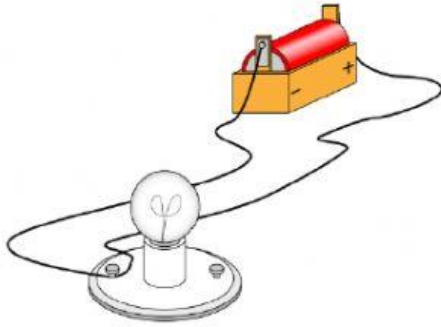

Did it work? **YES** **NO**

8. Will it work? **YES** **NO**

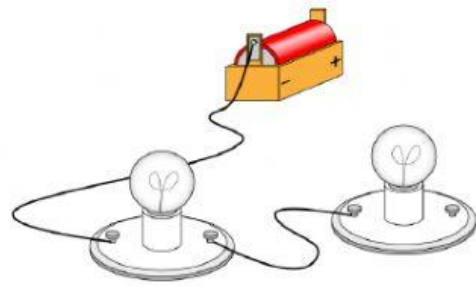

Did it work? **YES** **NO**

Green/Yellow/Red

I/S/L