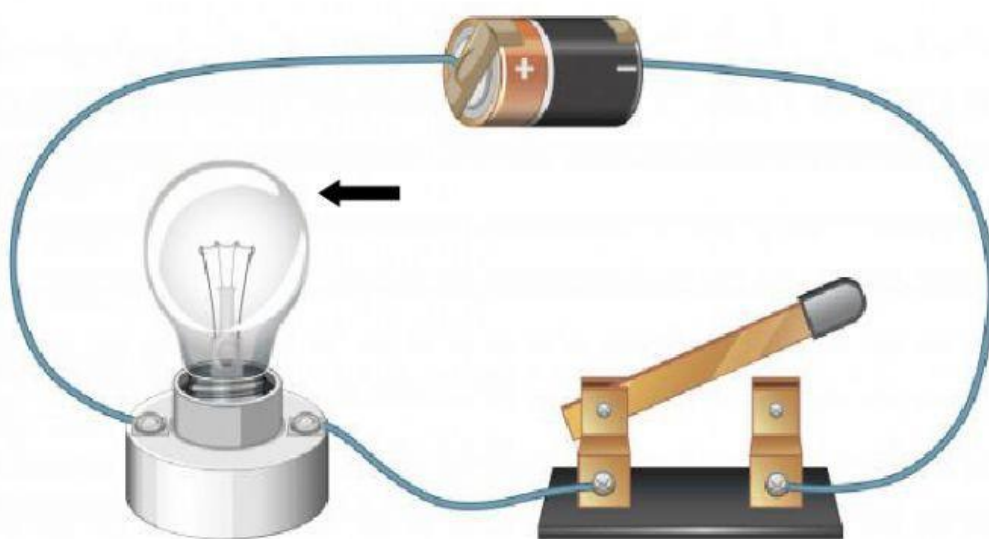


Match each word to the circuit.



bulb
switch
wire
cell
bulb holder

Match the name to the picture and the function.

wire



Turns the circuit on or off

buzzer



Moves something move

bulb



Stores the electricity

motor



Connects the parts of a circuit

cell



Lights up

switch



Makes a sound