

Date:

TOPIC: Using a switch


(1) Match part of the electric circuits below with their correct names.



light bulb holder



dry cell holder

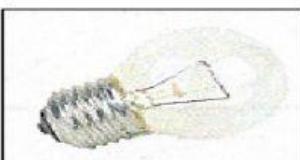

light bulb



wires



dry cell

(2) What happened when you turned the switch to the 'on' position? Why did this happen?

(3) What happened when you turned the switch to the 'off' position? Why did this happen?

(4) What is a switch used for?