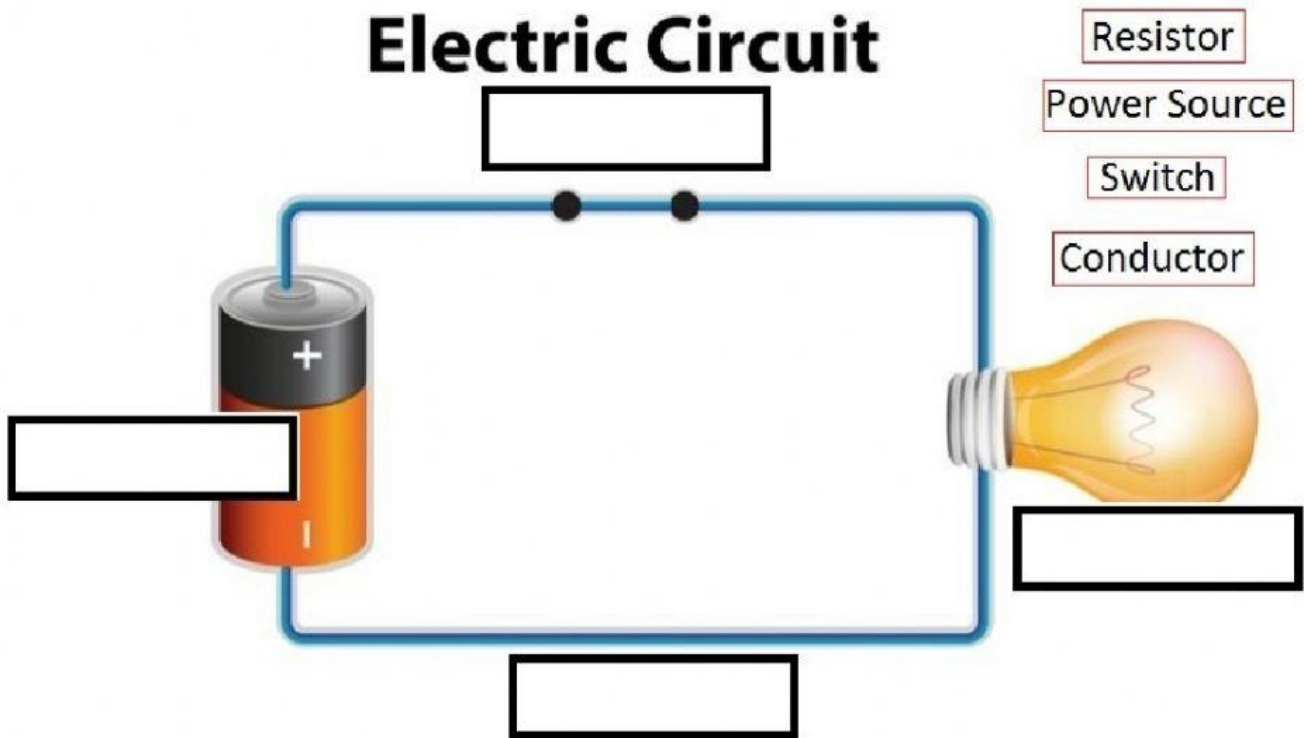


ELECTRICAL CIRCUIT

A) Drag and label the elements of the electrical circuit.



B) Match the elements to the definitions.

RESISTOR ●

CONDUCTOR ●

POWER SOURCE ●

SWITCH ●

● It generates the energy.

● It opens or closes the circuit.

● It converts electricity in another type of energy.

● Electricity flows through this element.