

# Chapter1: Section 1: Circuit construction

Your name:

Match:

Light-dependent resistors (LDR)




Resistor



Battery



Push button

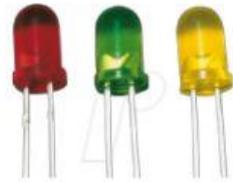

Potentiometer



Diode



