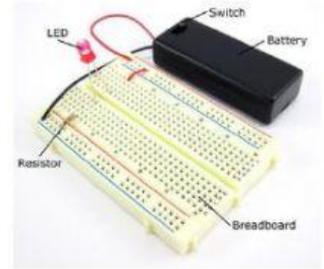


# Chapter1: Circuit construction

Label the figure below using the words below:

Name:



- 
- 
- 
- 

