

Name: \_\_\_\_\_

Date: \_\_\_\_\_

### **Electric circuit**

Answer the following questions.

1. Write down **three basic components** of an electric circuit.

a. \_\_\_\_\_

b. \_\_\_\_\_

c. \_\_\_\_\_

2. Dry cell is a \_\_\_\_\_ of electricity.

3. A switch is used to \_\_\_\_\_ or \_\_\_\_\_ an electric circuit.

4. The bulb will light up if the circuit is \_\_\_\_\_.

5. The bulb will not light up if the circuit is  
\_\_\_\_\_.