

SCIENCE WORKSHEET

1. What voltage do you need to make a 4 A current flow around a circuit with a resistance of 10 Ω ?

$$\begin{aligned}\text{voltage} &= \text{current} \times \text{---} \\ &= \text{---} \times \text{---} \\ &= \text{---} V\end{aligned}$$

Voltage = Current x Resistance

2. What is the resistance of a bulb when the voltage across it is 6 V and the current is 0.2 A?

$$\begin{aligned}\text{Resistance} &= \frac{\text{---}}{\text{---}} \\ &= \text{---} V\end{aligned}$$

You can use these formulae to calculate voltage, current or resistance.
voltage = current \times resistance
resistance = $\frac{\text{voltage}}{\text{current}}$
current = $\frac{\text{voltage}}{\text{resistance}}$