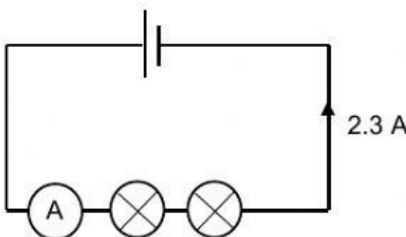
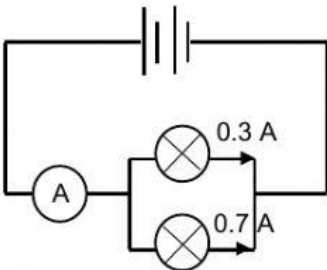
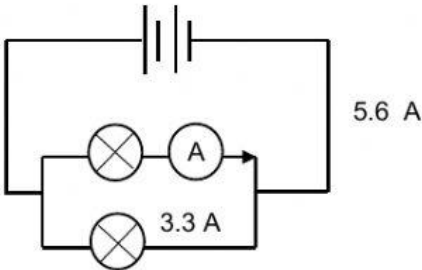
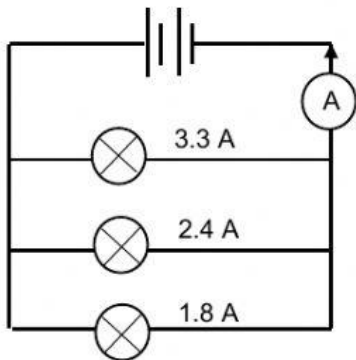


Name: ..... ( ) Class: ..... Date: .....

**LIVE Assignment 2: AMMETER READING**

	Circuit Diagram	Ammeter reading
(a)		
(b)		
(c)		

	Circuit Diagram	Ammeter reading
(d)		
(e)	<p>* please note that the two light bulbs are identical.</p> 