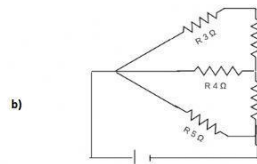





a) 



The diagram illustrates a circuit with a short circuit. A current source $i = 0$ is in parallel with a resistor $R_0 = 0$. The circuit also contains a $10\ \Omega$ resistor and a voltage source. A red 'X' marks the short circuit location, and the text "CIRCUITO CURTO" points to it.

a) 

b) 

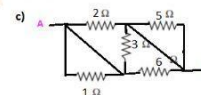

- a) 1
b) 2
c) 3
d) 4
e) 5

-