

Electrical Circuits



Activity 3

Theory



You programmed a microcontroller to complete an electric circuit in unit 2.


Label the components in the microcontroller that are used to make a simple electric circuit.

Use the list provided to help.

Connector to Power
source

Switch

Output light

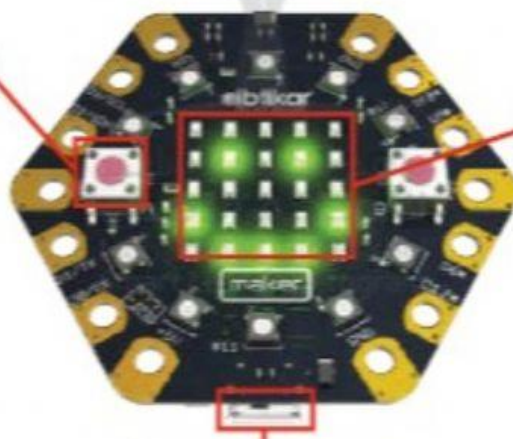

Student Feedback

S

T

R

E

A

M

Ai



48



LIVEWORKSHEETS