
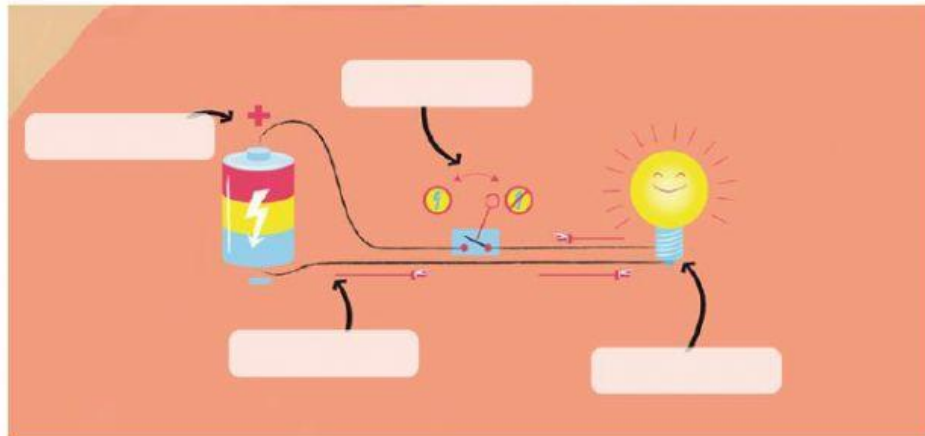


UNIT 6. ELECTRICITY. CURRENT ELECTRICITY

1. Label the electrical circuit.

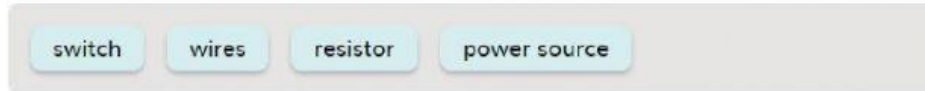

2. Match to make true sentences.

- | | | | |
|-----------------------|---|---|---|
| An electrical circuit | ● | ● | allows electrons to flow through a path. |
| Wires | ● | ● | transforms electricity into other forms of energy. |
| A resistor | ● | ● | opens and closes the circuit and can stop the flow of electricity |
| A power source | ● | ● | conduct electricity. |
| A switch | ● | ● | provides the electrical energy. |