

Parts of a circuit

Choose the name of the following images:

1. _



2. _



3. _



4. _



5. _



6. _



7. _

