

Write your name and your grade _____

Select the name of the following components



Lamp
Cable
Battery
resistor



Lamp
Cable
Switch
resistor



Lamp
Short circuit
Battery
cable



energy
bumb
Battery
cable




Lamp
Short circuit
light
cable




line
cable
switch
circuit

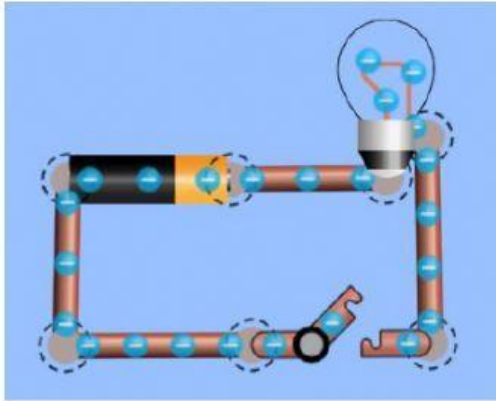
Select if the circuit are series circuit or parallel circuit



Series
parallel

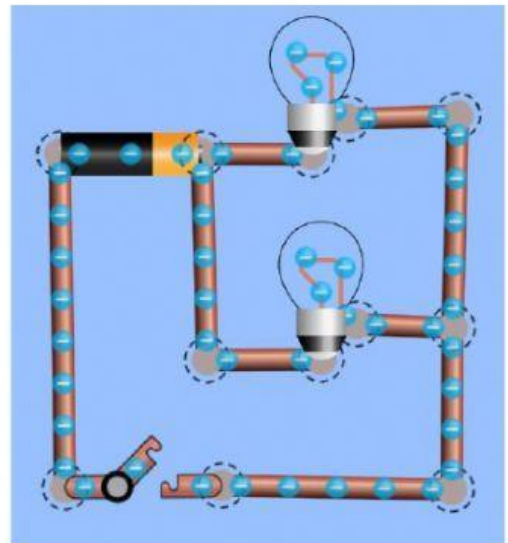

Series
parallel

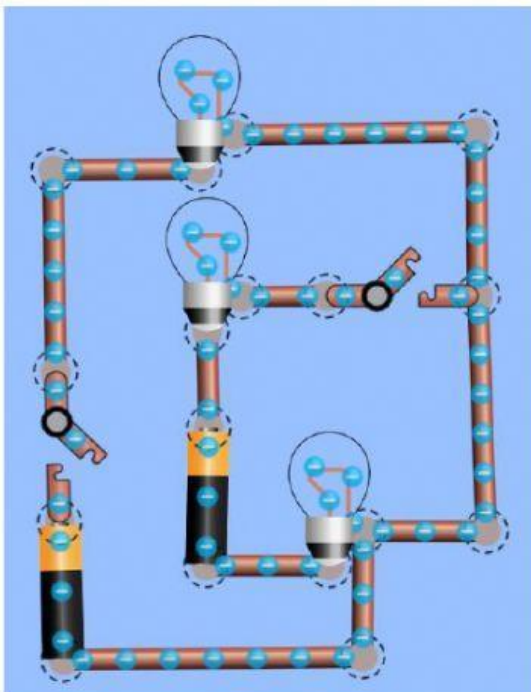

Series
parallel



Series
parallel