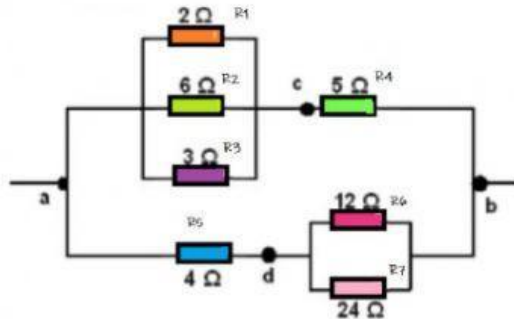



Completa el ejemplo paso a paso , completando los valores del circuito en el que estás trabajando :



$$I_1 =$$

$$I_2 =$$


$$I_3 =$$

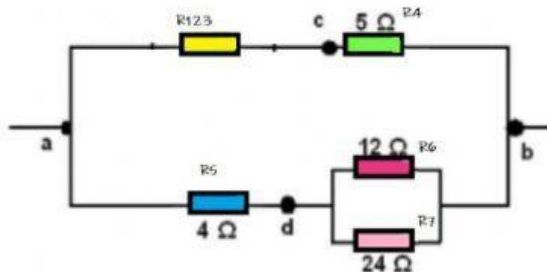

$$R_{123} =$$

$$I_{123} =$$

$$V_{123} =$$

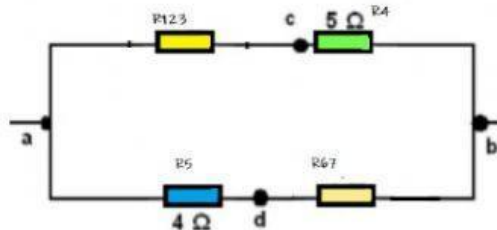


$$V_4 =$$

$$R_{67} =$$

$$V_5 =$$

$$V_{67} =$$

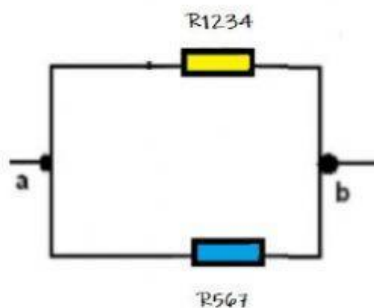


$$V_{1234} =$$

$$I_{1234} =$$

$$V_{567} =$$

$$I_{567} =$$

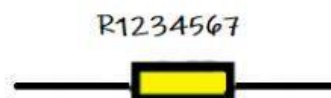

$$I_{total} =$$

20A 120 V 100V 8Ω 3,333A 80V 6,667A 10 A
 20A 30A 40V 20V 1Ω 120 V 120 V