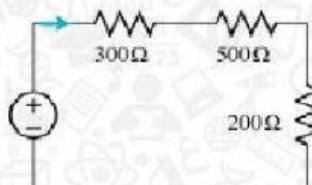


Total resistance

Activity 11

Theory

Calculate the total resistance of these resistors combination.



$$R = \boxed{\quad} \Omega$$

- S
- T
- R
- E
- A
- M

T