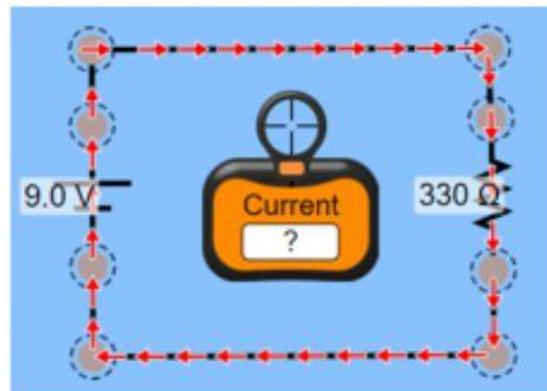


Image below shows part of an electronic circuit. Calculate the value of the current flow if the voltage is 9V and the resistor has a value of 330 ohms. Use the space below to show your working.

Hint: Use $V = I \times R$ to find the value of the current flow.



$$V = I \times R$$

$$I = V \div R$$

$$I =$$

|