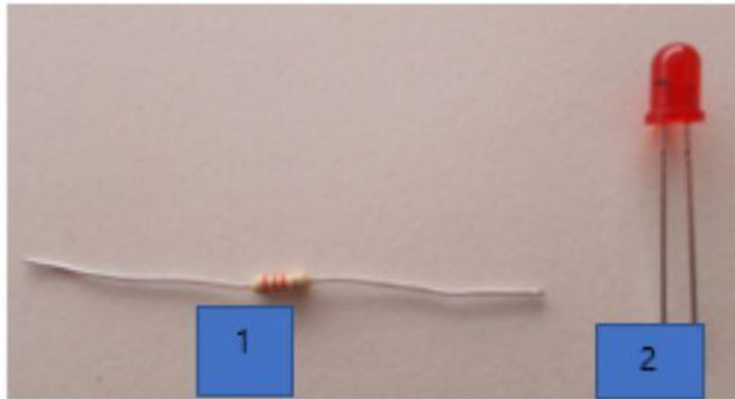




Activity 12

Image below shows a resistor and an LED. These two components are commonly used together in electronic circuits.



In the space below, draw the electronic symbol for a resistor and an LED.

