

Ahmed and Mariam are enjoying learning about circuits.

Help Ahmed to complete the activity that Mariam has created for him. ✓

**Write yes on the correct answer**

**Circuit image**

**Series circuit**

**Parallel circuit**

