

# 5th grade Science

## Electricity - Electric Circuits

When we talk about circuits there are 3 main types:

**Simple circuit**



**Series circuit**



**Parallel circuit**



Use the pictures to help you decide which circuit is being described.

1. Two or more lightbulbs are connected to one battery. \_\_\_\_\_
2. It forms two or more circles, one bigger than the other. \_\_\_\_\_
3. A battery is connected to a lightbulb, the lightbulb to a switch and the switch to the battery. \_\_\_\_\_
4. Each of these two circuits has a lightbulb, connected to the same battery.  
\_\_\_\_\_
5. All the components are connected within the same circuit. \_\_\_\_\_
6. This circuit has a single lightbulb and forms one circle. \_\_\_\_\_

