

Name: _____

Series and Parallel Circuits



Identify which of these circuits are parallel circuits and which are series circuits.













