
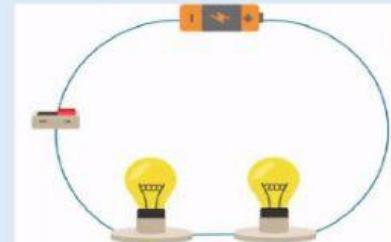


KENDRIYA VIDYALAYA KANNUR
LIVE WORKSHEET – TYPES OF CIRCUITS

NAME: _____

CLASS: _____

Drag & Drop

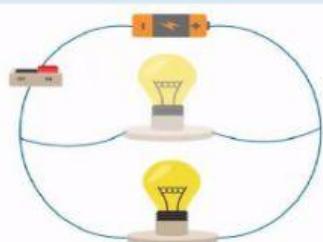

**AN EXAMPLE FOR
SERIES CIRCUIT IS**

**IN A PARALLEL CIRCUIT,
ALL THE ELECTRICAL
COMPONENTS ARE
CONNECTED ON AFTER
ANOTHER IN A
LOOP**

**AN EXAMPLE FOR
PARALLEL CIRCUIT IS**

**IN A SERIES CIRCUIT,
ALL THE ELECTRICAL
COMPONENTS ARE
CONNECTED ON AFTER
ANOTHER IN A
LOOP**

DECORATION LIGHTS

SERIES CIRCUIT

TWO OR MORE

SINGLE

PARALLEL CIRCUIT

HOUSE WIRING