
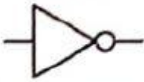
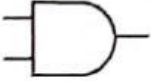
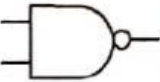
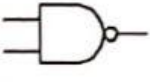
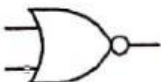


Logic gate	NAND equivalent circuit	NOR equivalent circuit
NOT 		
AND 		
NAND 		
OR 		
NOR 		

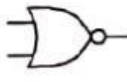Determine the truth tables for each of the logic gate circuits below. Then fit them into the right location in the table above.

