

Components of Circuit





Class-VII

Assignment-3

By:M.A.Shamsi

Bulb	Cell
Voltmeter	Closed circuit
Open switch	Battery
Resistor	Closed switch
Open circuit	Ammeter

Drag the correct name of each of the following electrical symbol in front of it:

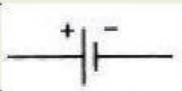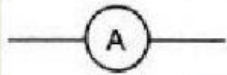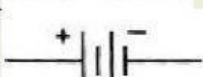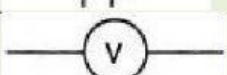1.		
2.		
3.		
4.		
5.		
6.		
7.		
8.		
9.		
10.	