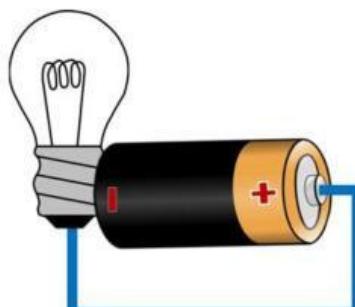


Worksheet time!




LA


Name the circuit below by filling in the blanks with complete or incomplete.



_____ circuit

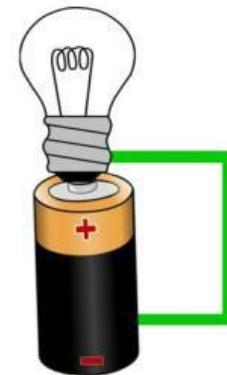


_____ circuit

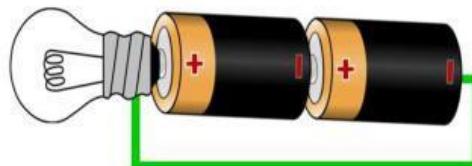

_____ circuit



_____ circuit

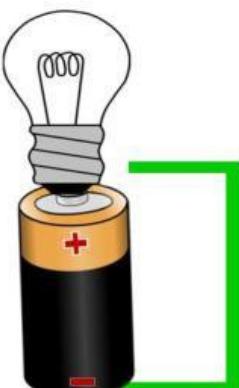

_____ circuit