

Worksheet time!



HA

A. Fill in the blank with the correct word.

complete	incomplete	not allow	allow	break	circuit
----------	------------	-----------	-------	-------	---------

Lightbulbs, dry cells and wires are basic component of a _____. When all the components are joined to each other, this will _____ electricity to flow through the circuit and causes the light bulbs to light up. This circuit is called a _____ circuit. But if the light bulbs do not light up, this maybe because there is a _____ in the circuit. This will _____ electricity to flow through the circuit. This circuit is called as an _____ circuit.

	6
--	---