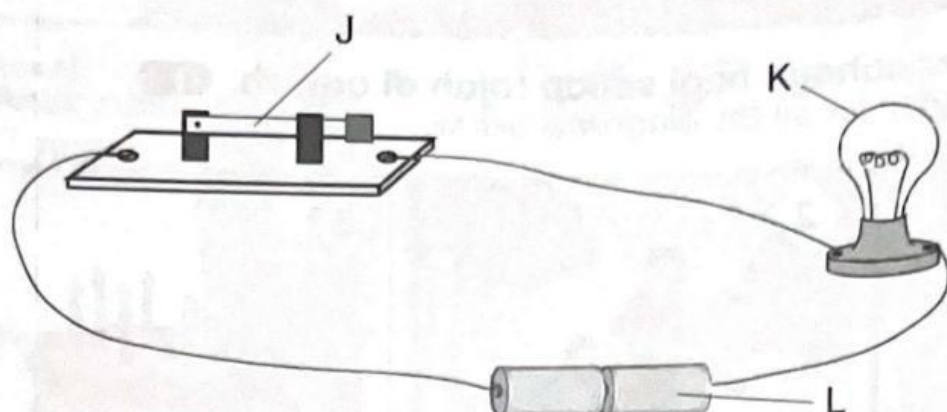


C Jawab soalan berdasarkan rajah di bawah.
 Answer the questions based on the diagram below.

TP 1 TP 2

[5 markah]
 [5 marks]



Mentol
 Mentol

Sel kering
 Dry cell

Suis
 Switch

1 Tuliskan huruf J, K dan L yang mewakili komponen elektrik.
 Write J, K and L that represent the electrical components.

2 (a) Labelkan komponen wayar penyambung dengan huruf M pada rajah atas.
 Label the connecting wire component with 'M' on diagram above.

(b) Apakah fungsi komponen M itu?
 What is the function of component M?

D Jawab semua soalan. **TP 5**
 Answer all the questions.

[5 markah]
 [5 marks]

1 Padankan.
 Match.

Membenarkan arus elektrik mengalir melaluinya
 Allows electric current to flow through it

Konduktor elektrik
 Electrical conductor

Tidak membenarkan arus elektrik mengalir melaluinya
 Does not allow electric current to flow through it

Penebat elektrik
 Electrical insulator




2 Berikan dua contoh penebat elektrik selain daripada di atas.
 Give two examples of electrical insulator besides the ones above.

B Jawab semua soalan yang berikut. TP 5

[12 markah]
[12 marks]

Answer all the following questions.

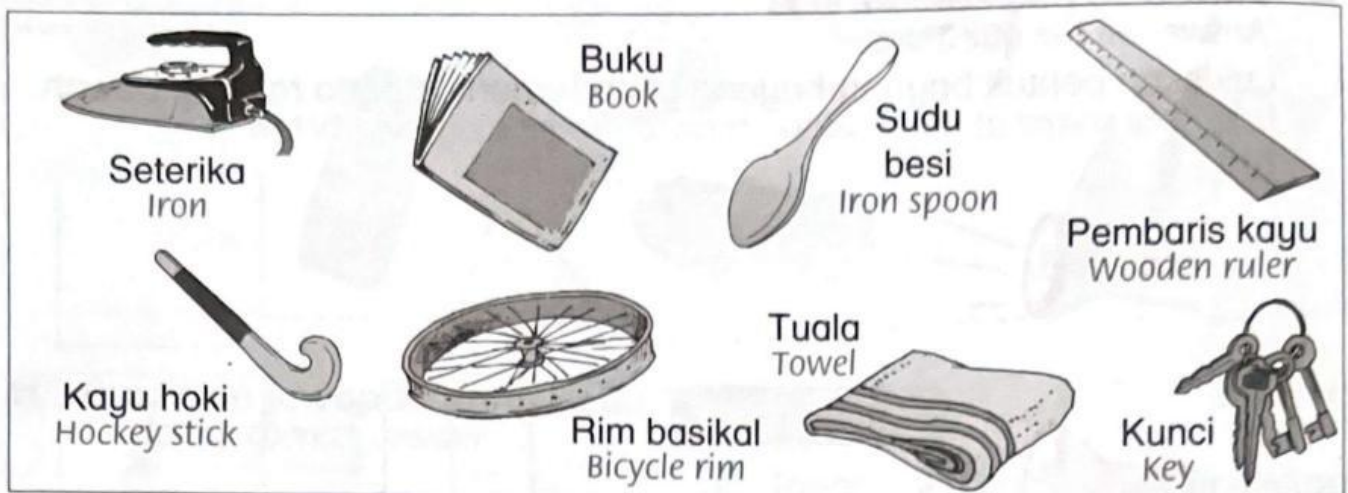- I** Kelaskan objek konduktor elektrik dan objek penebat elektrik.
Classify the electrical conductors and electrical insulators.



Konduktor elektrik
Electrical conductors

- (a) _____
(b) _____
(c) _____
(d) _____

Penebat elektrik
Electrical insulators

- (a) _____
(b) _____
(c) _____
(d) _____

- 2** Lengkapkan.
Complete these.

(a) Penebat elektrik ialah _____
Electrical insulators are _____

(b) Konduktor elektrik ialah _____
Electrical conductors are _____