

Name _____

Lets make electric circuits

What is an electric circuit?


A which allows to flow an
through it, is known as

electric circuit

system

electric current

Components of an electric circuit

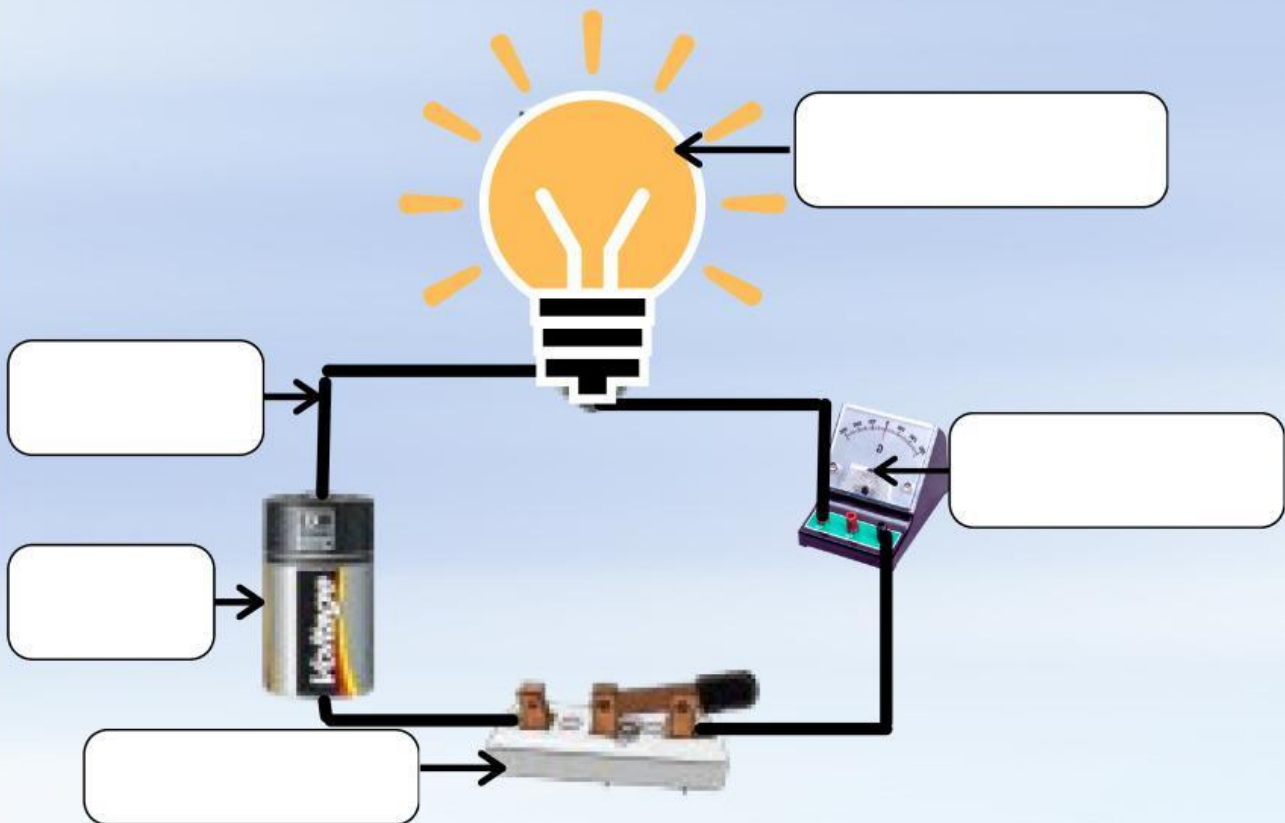

Wire


Bulb


Galvanometer

Dry cell

Switch

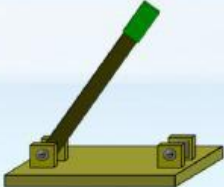Drag and drop the correct symbol of each component to the correct box



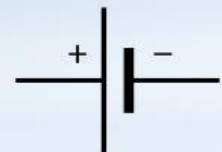Match the electric circuits to the correct circuit diagrams

