
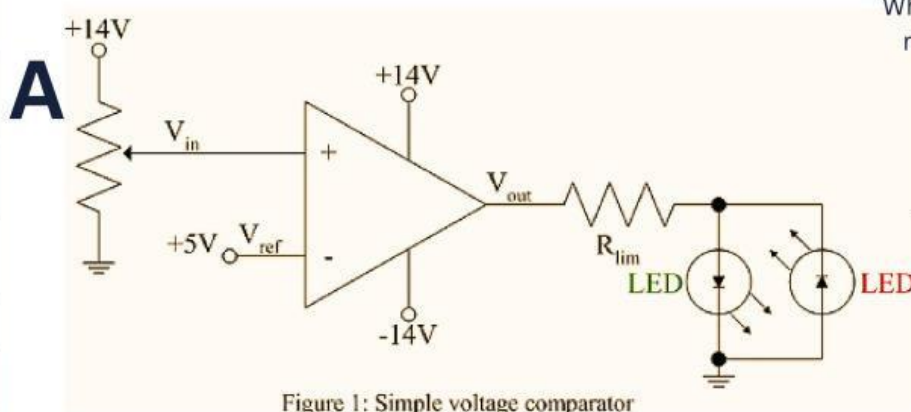
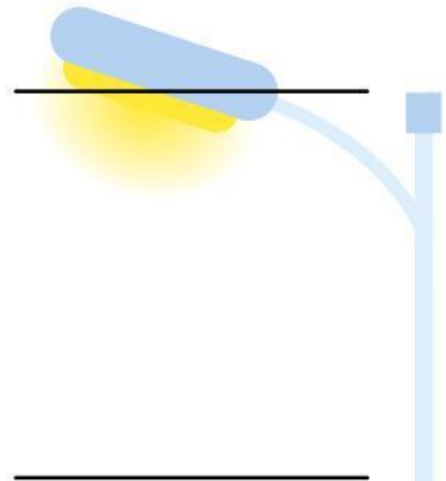


NAME:

COMPARATOR CIRCUITS

IDENTIFY WHERE THE BULB WILL BE LIT

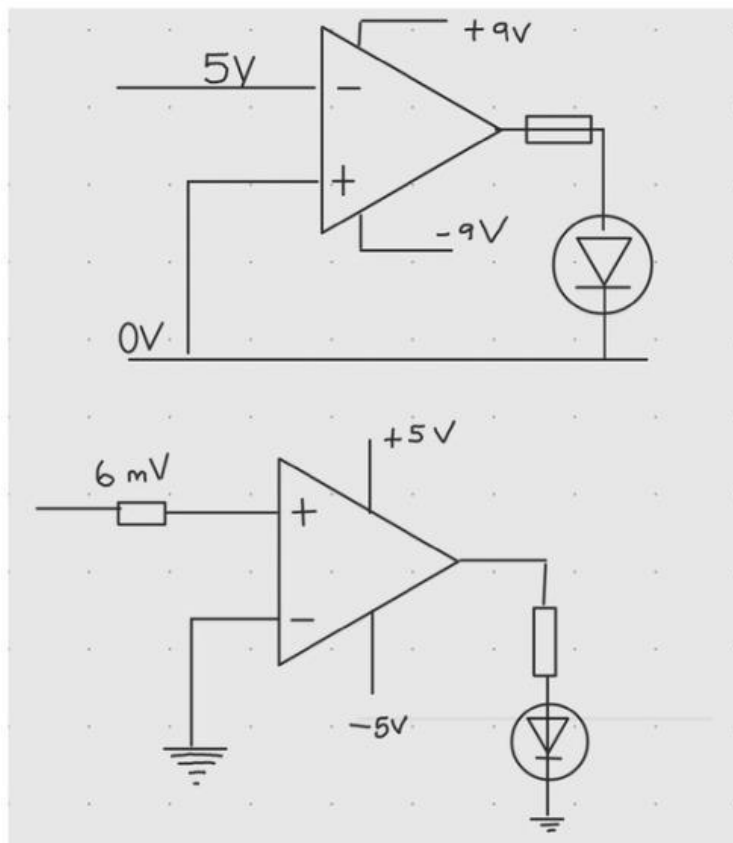

Which bulb, if any will light if V_{in} is read off from the middle of the potentiometer?

A
Picture Source