

Match the **statement** with the **correct name**.



Copyright © Ministry of Education – United Arab Emirates

Statement	Circuit type
Current divides when it reaches each branch.	Series circuit
Current flows on the same path.	
If one device in a breaks, it will not affect the rest of the devices from working.	
There is only one pathway.	
Adding branches does not affect the current available for each branch.	
The amount of current for each device is reduced when more devices are added to a series circuit.	Parallel circuit
There can be many pathways.	
If one device breaks, the whole circuit will not work.	
Current moves through one device and then through the next.	
The current is split into separate paths	