







Activity 4

Name: _____

Grade: _____

Rank these circuits below.

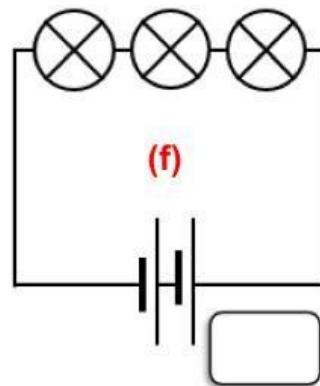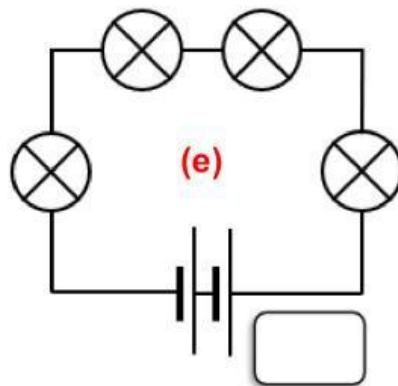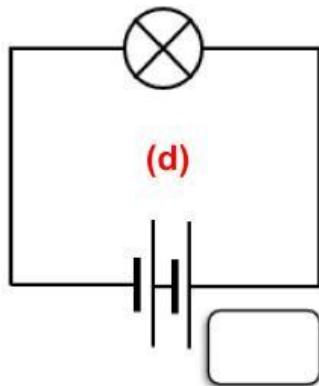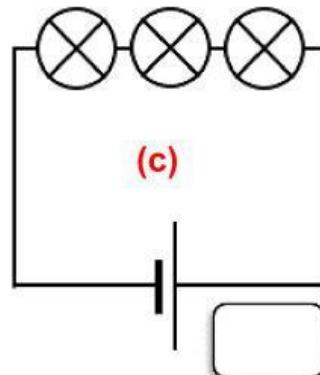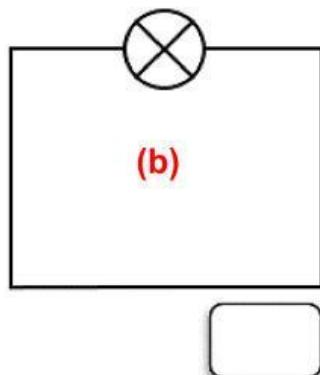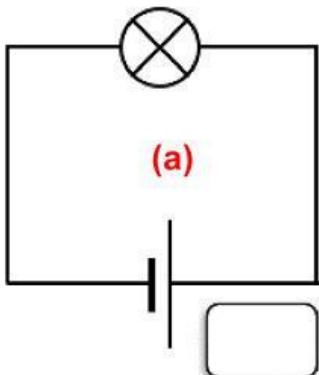Starting with the **brightest** bulb and ending with the **dullest** bulb.



Give a reason(s) to your answer.