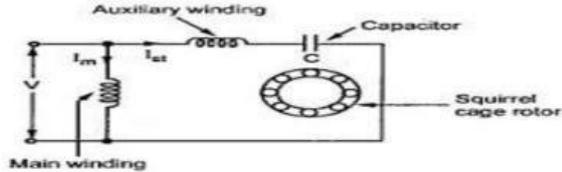
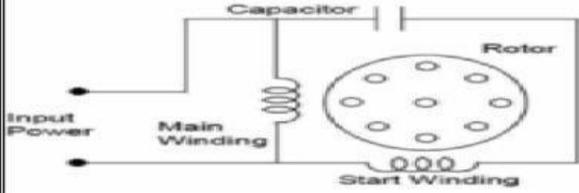
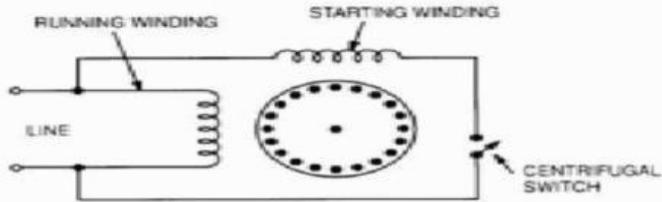
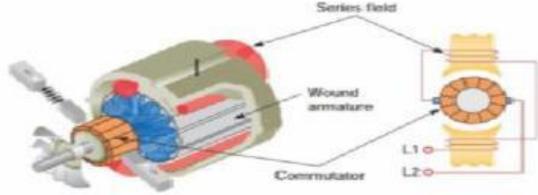
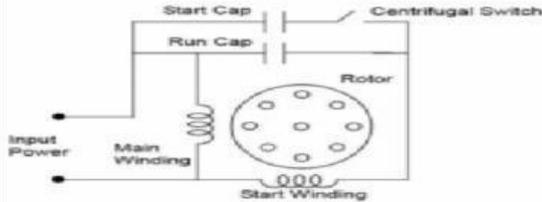


شعبة:

الرقم الاكاديمي:-

اسم الطالب:-

In the table shown ,match the picture with the appropriate motor shown?

No	Words	Picture
1-	Split phase motor	
2-	Capacitor start motor	
3-	Capacitor run motor	
4-	Capacitor start Capacitor run motor	
5-	Universal motor	

Teacher: AHMED SHAHIN

HEAD OF SECTION: REDHA HADI

HEAD MASTER: SAYED REDA